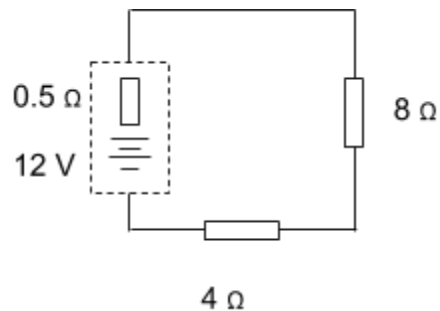


Non-Ideal Circuit Elements


1. A circuit is wired as shown. The battery has internal resistance $0.5\ \Omega$ and EMF $12\ \text{V}$.
 - a. Calculate the current in the circuit.
 - b. Determine the terminal voltage of the battery.
 - c. Calculate the power dissipated by the internal resistance of the battery.
 - d. Describe the effect this power dissipation would have on the battery.




2. An ideal $12\ \text{V}$ battery is wired in series with an ammeter, $18\ \Omega$, and $6\ \Omega$ resistor.
 - a. Draw the circuit diagram.
 - b. Calculate the current read by the ammeter if it is ideal.
 - c. Now assume the ammeter is non-ideal, and has an internal resistance of $0.5\ \Omega$. Calculate the effective resistance of this circuit and the current reading for the ammeter.

3. Given the circuit diagram.

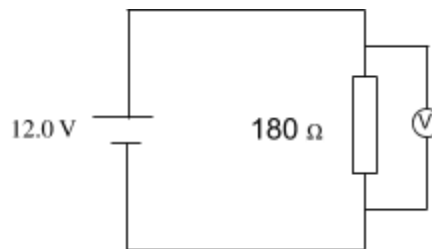
- a. Determine the voltage read by the voltmeter if it is ideal.
- b. Calculate the current through the $180\ \Omega$ resistor and the voltmeter.
- c. Now assume the voltmeter is non-ideal, and has an internal resistance of $1000\ \Omega$. Calculate the new effective resistance of this circuit and determine the voltage read by the voltmeter.
- d. Calculate the current through the $180\ \Omega$ resistor and the voltmeter.
- e. Describe the effect on the current of using a voltmeter that has a larger resistor.



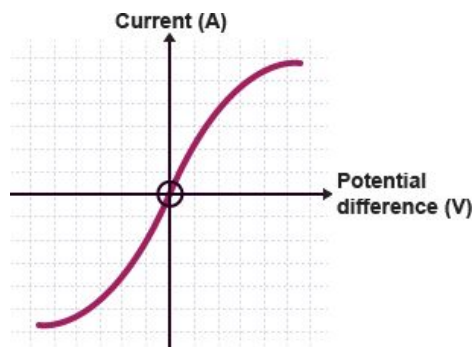4. The current vs voltage graph for a tungsten filament bulb is given on the right.
 - a. Determine how the resistance of the filament changes with voltage.
 - b. Explain how this is different than the resistors you have encountered.
 - c. What physical property of the filament may cause this behavior?



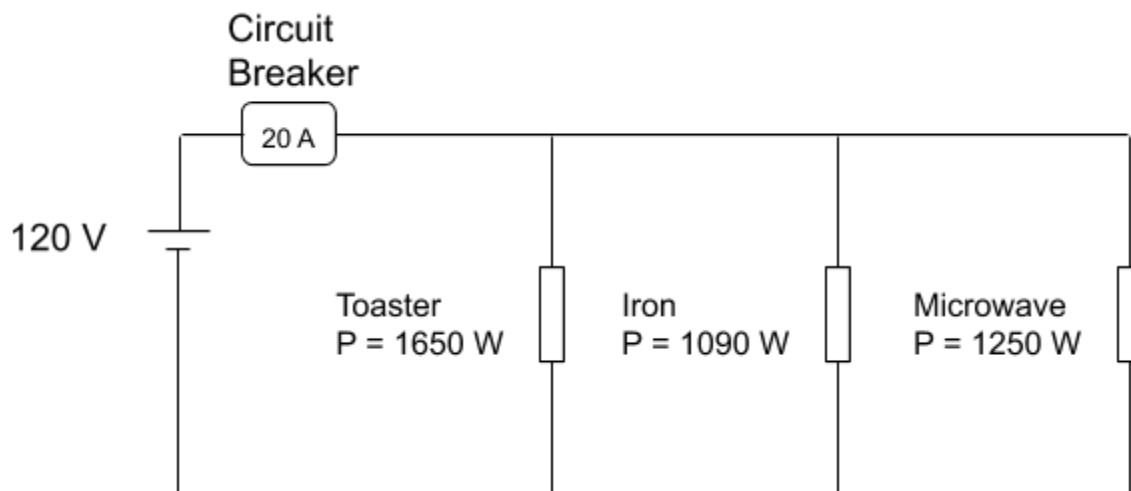5. A student wants to measure the current through a $3300\ \Omega$ resistor wired to a $10\ \text{V}$ power supply. The student accidentally uses the ammeter in parallel rather than series. Assume the ammeter has an internal resistance of $0.5\ \Omega$.
- Draw the circuit diagram.
 - Calculate the current that flows through the ammeter.
 - In the ammeter, there is a fuse designed to break at $0.5\ \text{A}$ of current. Does the fuse break?
 - Explain why the fuse is designed to break.
6. Circuit breakers are resettable automatic switches that open when a given current value is exceeded. A $1650\ \text{W}$ toaster, $1090\ \text{W}$ iron, and a $1250\ \text{W}$ microwave oven are turned on in a kitchen. As the drawing shows, they are all through a $20\ \text{A}$ circuit breaker to a $120\ \text{V}$ power supply.



- Obtain the total current delivered by the power supply if all three devices are used at the same time and determine if the circuit breaker will open.
- Explain the purpose of the circuit breaker.
- Compare a circuit breaker and a fuse.