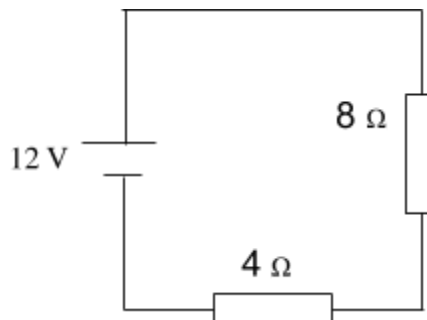



## Series and Parallel

1. A circuit is set up as shown.


- a. Calculate the effective resistance of the circuit.
- b. Calculate the current through the  $8\ \Omega$  resistor.
- c. Calculate the current through the  $4\ \Omega$  resistor.
- d. Calculate the potential difference across each resistor.



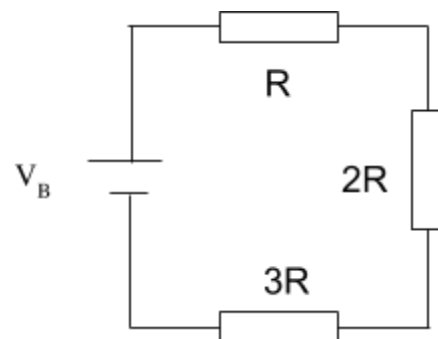2. Given the circuit shown with three resistors of  $R$ ,  $2R$ , and  $3R$  connected to an ideal battery with a potential difference of  $V_B$ . Calculate the potential difference across each resistor.




3. Consider this circuit.

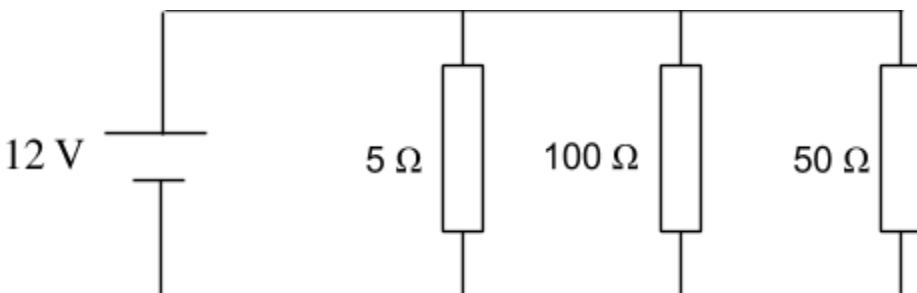

- a. Calculate the effective resistance of the circuit.
  - b. Calculate the current in each resistor.
  - c. Predict the effect on the circuit if another  $50\ \Omega$  resistor was added in parallel.
4. A circuit with three resistors of  $5\ \Omega$ ,  $6\ \Omega$ , and  $12\ \Omega$  is wired in parallel with an ideal battery with a potential difference of  $12\ \text{V}$ .
- a. Draw the circuit diagram.
  - b. Calculate the current through each resistor.
  - c. Calculate the current out of the battery.

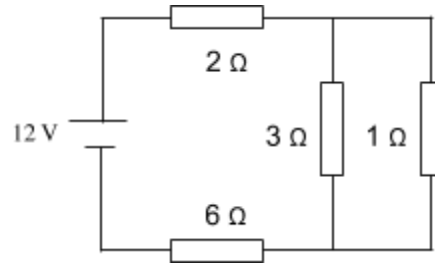
5. Consider this circuit.

- Calculate the effective resistance of the circuit.
- Calculate the voltage across each resistor.
- Calculate the current through each resistor.
- Calculate the power dissipated by each resistor.
- Predict the effect on the circuit if the  $3\ \Omega$  resistor was replaced with a  $100\ \Omega$  resistor.
- Predict the effect on the circuit if the  $6\ \Omega$  resistor was replaced with a  $100\ \Omega$  resistor.



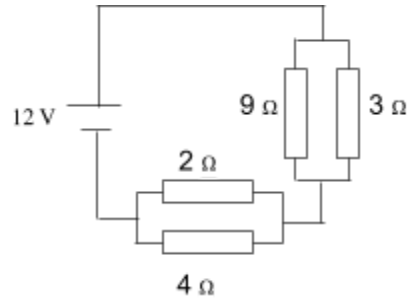6. Consider this circuit.

- Calculate the effective resistance of the circuit.
- Calculate the voltage across each resistor.
- Calculate the current through each resistor.
- Calculate the power dissipated by each resistor.



7. Consider this circuit.

- Calculate the effective resistance of the circuit.
- Calculate the voltage across each resistor.
- Calculate the current through each resistor.
- Calculate the power dissipated by each resistor.
- Predict the effect on the circuit if the  $3\ \Omega$  resistor was replaced with a  $100\ \Omega$  resistor.
- Predict the effect on the circuit if the  $6\ \Omega$  resistor was replaced with a  $100\ \Omega$  resistor.

