

Derivation of Capacitor Charging and Discharging Equations

Charging of a Capacitor (Switch in Position A)

By Kirchhoff's Laws, $V_B - V_R - V_C = 0$. With some simple substitution, $V_B - iR - \frac{q}{C} = 0$. We know that the current describes the rate at which charge is increasing on the plate of the capacitor. This can be written as $i = \frac{dq}{dt}$.

This leads to $V_B - \frac{dq}{dt}R - \frac{q}{C} = 0$

With some algebra, this equation becomes

$$\frac{V_B C - q}{RC} = \frac{dq}{dt}$$

Separating the variables of q and t gives $\frac{dt}{RC} = \frac{dq}{V_B C - q}$

This form can be analysed by assuming $u = V_B C - q$ which leads to $du = -dq$

So $\frac{dt}{RC} = -\frac{du}{u}$.

Integrating both sides $\int \frac{dt}{RC} = \int -\frac{du}{u}$ leads to $\frac{t}{RC} + k = -\ln(u)$ where k is some constant.

Substituting for u and multiplying by -1 leads to $-\frac{t}{RC} - k = \ln(V_B C - q)$

So $e^{-\frac{t}{RC}} e^{-k} = V_B C - q$ but we know that at $t=0$, $q=0$ so $e^{-k} = V_B C$

Then $V_B C e^{-\frac{t}{RC}} = V_B C - q$

Solving for q gives

$$q = V_B C (1 - e^{-\frac{t}{RC}})$$

which is the equation that describes the charge on a capacitor during charging.

Since the potential difference across the capacitor is $V = \frac{q}{C}$,

$$V_C = V_B (1 - e^{-\frac{t}{RC}})$$

As stated earlier, $i = \frac{dq}{dt}$ so $i = \frac{d}{dt}(V_B C (1 - e^{-\frac{t}{RC}})) = (-\frac{1}{RC})V_B C (-e^{-\frac{t}{RC}})$. This simplifies to:


$$i = \frac{V_B}{R} e^{-\frac{t}{RC}}$$

The resistor obeys Ohm's Law $V = iR$, so

$$V_R = V_B e^{-\frac{t}{RC}}$$

Notice that all of these equations include $e^{-\frac{t}{RC}}$. RC determines the rate of change for the curves. This is a quantity called the "time constant."

$$\tau = RC$$

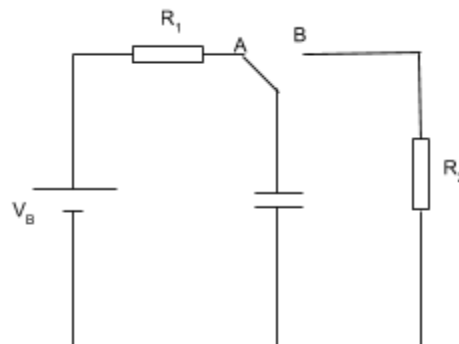

Discharging a Capacitor (Switch in Position B)

When the switch is changed from position A to position B, Kirchhoff's law gives $V_C - V_R = 0$.

Substituting $V_C = \frac{q}{C}$ and $V_R = iR$ leads to $\frac{q}{C} - iR = 0$.

During the discharge process, $i = -\frac{dq}{dt}$ so

$$\frac{q}{C} - \left(-\frac{dq}{dt}\right)R = 0.$$

Separating variables $-\frac{dt}{RC} = \frac{dq}{q}$.

Integrating both sides $\int -\frac{dt}{RC} = \int \frac{dq}{q}$ leads to $-\frac{t}{RC} + k = \ln(q)$ and $e^{-\frac{t}{RC}} e^k = q$

Knowing that at $t=0$, $q=q_0$ produces the equation

$$q = q_0 e^{-\frac{t}{RC}}$$

Since $i = -\frac{dq}{dt}$ and $q_0 = CV_0$

$$i = \frac{V_0}{R} e^{-\frac{t}{RC}}$$

Going back to Ohm's law and Kirchhoff's law

$$V_C = V_R = V_0 e^{-\frac{t}{RC}}$$

