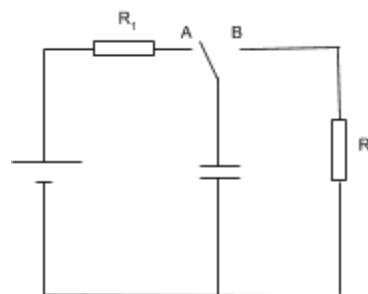


## **Capacitor Structure Practice Problems**

1. Calculate the voltage required to store  $7.2 \times 10^{-5}$  C of charge on a  $6.0 \mu\text{F}$  capacitor.
2. A parallel plate capacitor has a capacitance of  $10 \mu\text{F}$ .
  - a. Determine the capacitance if the area doubles.
  - b. Determine the capacitance if the spacing between doubles.
  - c. Determine how the capacitance will change if the dielectric between the plates is doubled.
3. A parallel plate capacitor of  $7.0 \mu\text{F}$  when filled with a dielectric. The area of each plate is  $1.5 \text{ m}^2$  and the separation between the plates is  $1.0 \times 10^{-5} \text{ m}$ . Calculate the dielectric constant of the dielectric.
4. A capacitor has a capacitance of  $2.5 \times 10^{-8} \text{ F}$ . In the charging process, electrons are removed from the positive plate and added to the negative plate. Determine the number of electrons transferred when the potential difference between the plates is  $45 \text{ V}$ .

5. In the circuit to the right, the ideal battery has a potential difference of  $6.0$  volts.  $R_1 = 1000 \Omega$  and  $R_2 = 100 \Omega$ . The capacitor has a capacitance of  $5.0 \mu\text{F}$ . The capacitor begins uncharged.



- a. What is the current out of the power supply when the switch is originally turned to the A position?
- b. Sketch the graph of the potential difference across  $R_1$  from the moment the switch is turned to the A position until much later.
- c. Sketch the graph of the potential difference across the capacitor from the moment the switch is turned to the A position until much later.
- d. How much energy is stored in the capacitor when it is fully charged?
- e. Calculate the current through  $R_2$  immediately after the switch is flipped to position B.
- f. Sketch the graph of the potential difference across  $R_2$  from the moment the switch is turned to the B position until much later.
- g. What happened to the energy that was stored in the capacitor?
- h. Compare the time to charge the capacitor to the time to discharge. Explain your reasoning.