

DDP Physics

Capacitor Structure Practice Problems

1) $C = \frac{q}{V} \Rightarrow V = \frac{q}{C} = \frac{7.2 \times 10^{-5}}{6.0 \times 10^{-6}} = \boxed{12 \text{ V}}$

2) $C_1 = \epsilon \frac{A_1}{d_1}$ a) If $A_2 = 2A_1$, $C_2 = \epsilon \frac{(2A_1)}{d_1} = \boxed{2C_1}$

b) If $d_3 = 2d_1$, $C_3 = \frac{\epsilon_1 A_1}{2d_1} = \boxed{\frac{C_1}{2}}$

c) If $\epsilon_2 = 2\epsilon_1$, $C_4 = \frac{(2\epsilon_1) A_1}{d_1} = \boxed{2C_1}$

3) $C = \epsilon \frac{A}{d} \Rightarrow C = \kappa \epsilon_0 \frac{A}{d} \Rightarrow \kappa = \frac{C d}{\epsilon_0 A} = \frac{(7.0 \times 10^{-6})(1 \times 10^{-5})}{(8.85 \times 10^{-12})(1.5)}$
 $\boxed{\kappa = 5.27}$

4) $C = \frac{q}{V} \Rightarrow q = CV = (25 \times 10^{-9})(45) = 1.125 \times 10^{-6} \text{ C}$
 $(1.125 \times 10^{-6} \text{ C}) \left(\frac{1 e^-}{1.6 \times 10^{-19} \text{ C}} \right) = \boxed{7.03 \times 10^{12} e^-}$




5) If switch is in position A $V_B - V_R - V_C = 0$

a) @ $t=0$ $V_C = 0 \Rightarrow 6 - iR_1 - 0 = 0$

$6 - i(1000) = 0 \Rightarrow \boxed{i = 6 \times 10^{-3} \text{ A}}$

starts @ 6V and decreases to 0V

starts @ 0V and increases to +6V

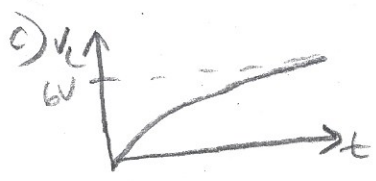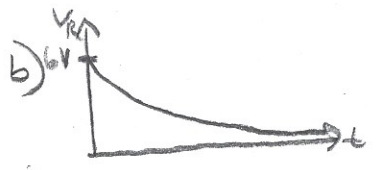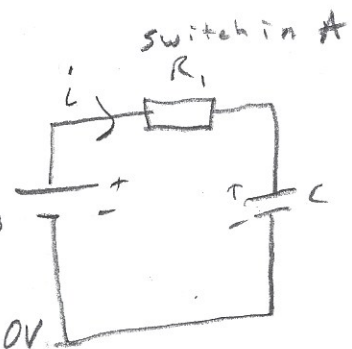

$\tau_1 = R_1 C = (1000)(5 \times 10^{-6}) = 5 \times 10^{-3} \text{ s}$

d) $E = \frac{1}{2} CV^2 = \frac{1}{2} (5 \times 10^{-6})(6)^2 = \boxed{9 \times 10^{-5} \text{ J}}$



5) cont. e) $V_C - V_R = 0$

@ $t=0$ $V_C = 6V$

$6 - iR_2 = 0$

$6 - i(100) = 0$

$i = 6 \times 10^{-2} A$

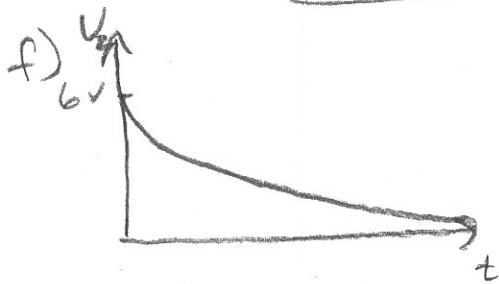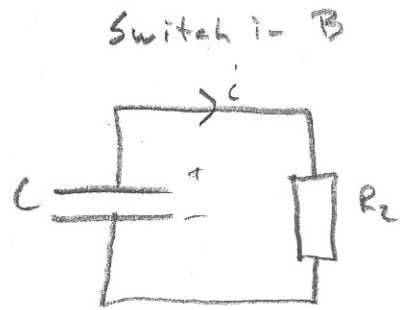

Starts @ 6V and decays to 0V

g) Energy is converted to heat by the resistor.

h) $\tau_B = R_2 C = (100)(5 \times 10^{-6}) = 5 \times 10^{-4} s$

compare time to $\frac{V}{2}$ or 3V using $V = V_0 e^{-\frac{t}{\tau}}$

Switch is A
 $\tau_A = 5 \times 10^{-3} s$

$3 = 6 e^{-\frac{t}{(5 \times 10^{-3})}} \Rightarrow 0.5 = e^{-\frac{t}{(5 \times 10^{-3})}} \Rightarrow -\ln(0.5) = \frac{t_A}{5 \times 10^{-3}}$

$t_A = 0.0035 s$

Switch is B
 $\tau_B = 5 \times 10^{-4} s$

$3 = 6 e^{-\frac{t_B}{(5 \times 10^{-4})}} \Rightarrow 0.5 = e^{-\frac{t_B}{5 \times 10^{-4}}} \Rightarrow -\ln(0.5) = \frac{t_B}{5 \times 10^{-4}}$

$t_B = 0.00035 s$

The time to half charge $t_{\frac{1}{2}A} = 10 t_{\frac{1}{2}B}$. It would take 10x as long to charge as to discharge.

(For an application, look up the flash on a camera)